




Course Title: Control Systems – sec.1	Date: 24/3/2019
Course No: (610414+640344)	Time Allowed: 50 minutes
Lecturer: Dr. Mohammed Mahdi	No. of Pages: 1

**Question 1:**

(50 Marks)

**Objectives:** This question is about the electrical analogy RLC circuit.

Given the following RLC circuit.

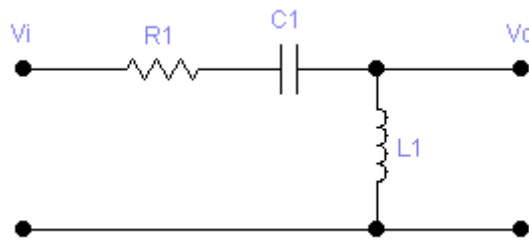

It is required to :-


1. Prove that the transfer function  $\frac{Vo(s)}{Vi(s)} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$  (20 marks)
2. Define circuit characteristics. (10 marks)
3. System differential equation. (10 marks)
4. Calculate  $Vo(0)$ ,  $Vo(\infty)$  for  $Vi$  = unit impulse change in input. (10 marks)

**Question 2:**

(50 Marks)

**Objectives:** This question is about closed loop control system

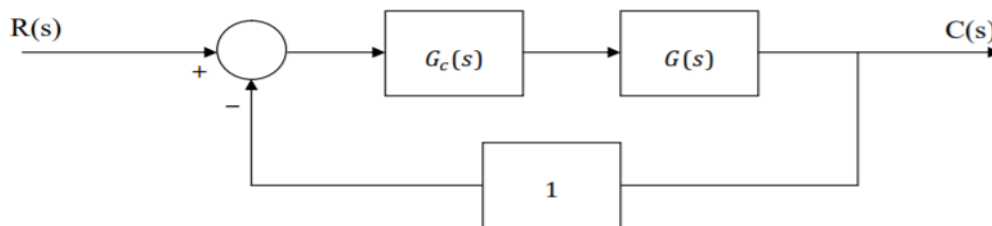Given the following general negative feedback control system block diagram.



If controller  $G_c(s) = k$ , feedback  $H(s) = 1$ , and process  $G(s) = \frac{5}{s^2 + 10s + 5}$ , it is required to:-

1. Calculate closed loop transfer function. (10 Marks)
2. Show kinds of system's responses as a function of k. (10 Marks)
3. System's parameters for  $k = 4$ . (10 Marks)
4.  $C(t)$  for  $k = 4$ , and input is unit step change. (20 Marks)